

P1). 3-Bit upcounter

Design code:

```
module counter(input clk, rst, output reg
[2:0]count);
  reg [2:0]temp;

  always@(posedge clk )begin
    if(rst)
      temp <= 3'b0;
    else
      temp <= temp + 1;
  end
  assign count = temp;
endmodule
```

Test bench code:

```
module tb;
  reg clk, rst;
  wire [2:0]count;

  counter dut(clk, rst, count);


  always #5 clk = ~clk;

  initial begin
    clk = 0;
    rst = 1;
    #10 rst = 0;
    $monitor("count = %0b", count);
    #50 finish;
  end

  initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0, clk, rst, count);
  end
endmodule
```

OUTPUT:
 
```
reset = 0, count = 0
reset = 0, count = 1
reset = 0, count = 10
reset = 0, count = 11
reset = 0, count = 100
reset = 0, count = 101
reset = 0, count = 110
reset = 0, count = 111
reset = 0, count = 0
reset = 0, count = 1
reset = 0, count = 10
reset = 0, count = 11
```



P2). 3-Bit down counter

Design code:

```
module counter(input clk, rst,
output [2:0]count);
reg [2:0]temp;

always@(posedge clk )begin
    if(rst)
        temp <= 3'd7;
    else
        temp <= temp - 1;
end
assign count = temp;
endmodule
```

Test bench code:

```
module tb;
    reg clk, rst;
    wire [2:0]count;


    counter dut(clk, rst, count);

    always #5 clk = ~clk;
    initial begin
        clk = 0;
        rst = 1;
        #10 rst = 0;
        #100 rst = 1;
        #50 rst = 0;
        $monitor("reset = %0b, count = %0b", rst,count);
        #200 $finish;
    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(0, clk, rst, count);
    end
endmodule
```

OUTPUT:
 
```
reset = 0, count = 111
reset = 0, count = 110
reset = 0, count = 101
reset = 0, count = 100
reset = 0, count = 11
reset = 0, count = 10
reset = 0, count = 1
reset = 0, count = 0
reset = 0, count = 111
reset = 0, count = 110
reset = 0, count = 101
reset = 0, count = 100
```



P3). 3- bit updown counter

Design code:

```
module counter(input clk, rst, up, output
[2:0]count);
  reg [2:0]temp;
  assign count = temp;
  always @(posedge clk) begin
    if (rst)
      temp <= 3'b000;
    else begin
      if (up)
        temp <= temp + 1;
      else
        temp <= temp - 1;
    end
  end
end
endmodule
```

Test bench code:


```
// Code your testbench here
// or browse Examples
module tb;
  reg clk, rst, up, down;
  wire [2:0]count;

  counter dut(clk, rst, up, count);

  always #5 clk = ~clk;
  initial begin
    clk = 0;
    rst = 1;
    up = 1;
    #10 rst = 0;
    up = 1;
    #100
    up = 0;
    $monitor("count = %0b", count);
    #500 $finish;
  end

  initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0, clk, rst, up, count);
  end
endmodule
```

OUTPUT:

 

P4). Ring counter

Design code:

```
module counter(input clk, rst, output
[3:0]out);
  reg [3:0]temp;

  always@(posedge clk )begin
    if(rst)
      temp <= 4'b1110;//declare with non zero
value
    else
      temp <= {temp[0], temp[3:1]};
  end
  assign out = temp;
endmodule
```

Test bench code:


```
module tb;
  reg clk, rst;
  wire [3:0]out;

  counter dut(clk, rst, out);

  always #5 clk = ~clk;
  initial begin
    clk = 0;
    rst = 1;
    #10 rst = 0;
    #100 rst = 1;
    #50 rst = 0;
    $monitor("reset = %0b, out = %0b",
rst,out);
    #200 $finish;
  end

  initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0, clk, rst, out);
  end
endmodule
```

OUTPUT:

 

P4). Johnson counter

Design code:

```
module counter(input clk, rst, output
[3:0]out);
    reg [3:0]temp;

    always@(posedge clk )begin
        if(rst)
            temp <= 4'b1110;//declare with non zero
value
        else
            temp <= {~temp[0], temp[3:1]};
    end
    assign out = temp;
endmodule
```

Test bench code:


```
module tb;
    reg clk, rst;
    wire [3:0]out;

    counter dut(clk, rst, out);

    always #5 clk = ~clk;
    initial begin
        clk = 0;
        rst = 1;
        #10 rst = 0;
        #100 rst = 1;
        #50 rst = 0;
        $monitor("reset = %0b, out = %0b",
rst,out);
        #200 $finish;
    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(0, clk, rst, out);
    end
endmodule
```

OUTPUT:

 

P5). Gradually incrementing and decrementing counter

<i>Design code:</i>	<i>Test bench code:</i>

OUTPUT:

KVLS/2501091

KVLS/2501091